

# Solving Logic Problems using Truth Tables

---

# Solving Logic Problems using Truth Tables

---

Defining a Logic Problem

Selecting and Using an appropriate Truth Table

Using Truth Tables to determine the solution to a Logic Problem

Implementing the solution using hardware (engineering)

Implementing the solution using software (computer science)

# Defining a Logic Problem

---

The assumption for this lesson is that a logic problem consists of

- Binary inputs – all inputs are yes/no, on/off, or true/false inputs
- Binary outputs – the output(s) are yes/no, on/off, or true/false
- The state of the output is based on the state of the inputs

Example: If the burglar alarm is engaged and a window is open or motion is detected, sound the alarm.

# Identify the Inputs and Outputs

---

For each input and output, identify what constitutes on and off (true and false).

Example: If the burglar alarm is turn on and a window is open or motion is detected, sound an audible alarm.

## Inputs

- Burglar Alarm: 1 – Alarm On, 0 – Alarm Off
- Window: 1 – Closed, 0 – Open
- Motion Detector: 1 – Motion, 0 – No Motion

## Outputs

- Alarm: 1 – On, 0 – Off

# Select an appropriate Truth Table

The appropriate Truth Table is based on the number of inputs

**Two Inputs**

X	Y	Out
0	0	
0	1	
1	0	
1	1	

**Three Inputs**

X	Y	Z	Out
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

**Four Inputs**

W	X	Y	Z	Out
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

# Fill in the Truth Table

---

X	Y	Z	Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

X = Burglar Alarm: 1 – Alarm On, 0 – Alarm Off

Y = Window: 1 – Closed, 0 – Open

Z = Motion Detector: 1 – Motion, 0 – No Motion

Out = Alarm: 1 – On, 0 - Off

# Document the Solution

---

X	Y	Z	Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Identify the inputs that cause the output to be 1. These are the min-terms.

Write the equation for each min-term.

If an input is 1, write the variable name. If the input is 0, write the inverse of the variable name.

If X = 0, use  $\bar{X}$

If X = 1, use X

Inputs are AND'ed (the first min-term is  $X * \bar{Y} * \bar{Z}$ )

Combine min-terms to form the equation

Min-terms are OR'ed

The full solution is  $X\bar{Y}\bar{Z} + X\bar{Y}Z + XYZ$

# Simplify the Solution

---



Solutions can be simplified using Boolean Algebra or Karnaugh Mapping. These topics are beyond the scope this lesson, therefore this lesson will use unsimplified logic expressions.



# Test the Solution (Hardware)

$$X\bar{Y}\bar{Z} + X\bar{Y}Z + XYZ$$

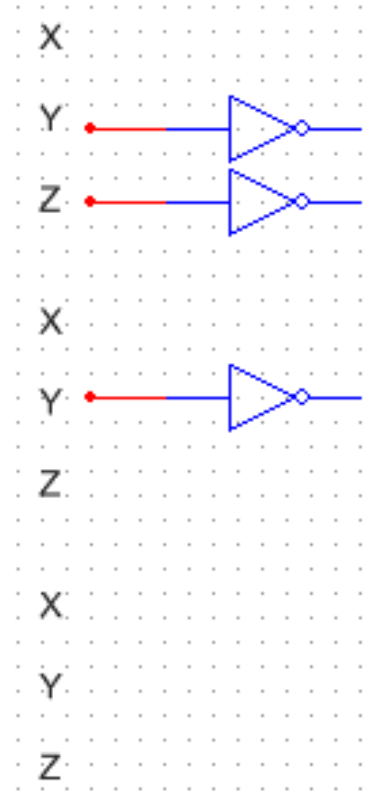
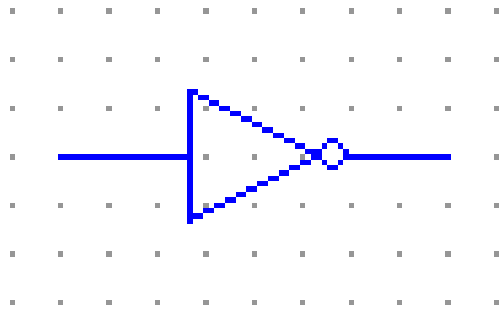
- 1) Invert any inputs that have to be inverted using an Inverter Gate



# Test the Solution (Hardware)

$$X\bar{Y}\bar{Z} + X\bar{Y}Z + XYZ$$

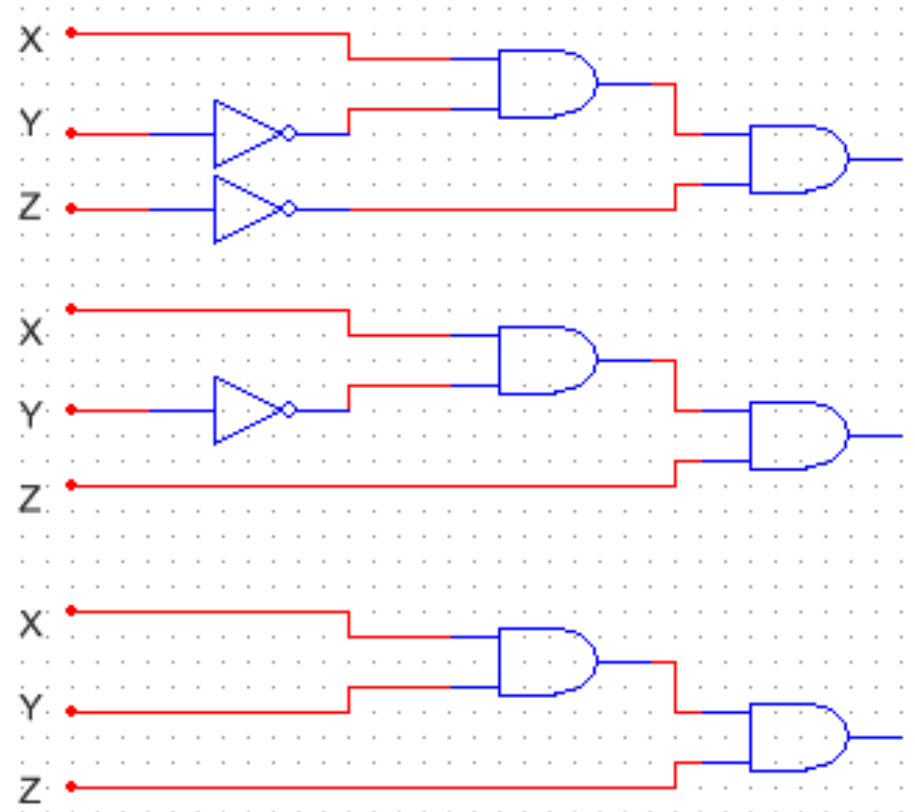
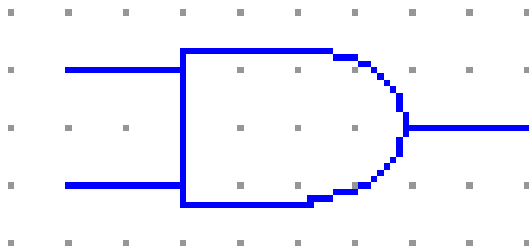
- 2) AND the inputs to form a min-term using an AND Gate



# Test the Solution (Hardware)

$$X\bar{Y}\bar{Z} + X\bar{Y}Z + XYZ$$

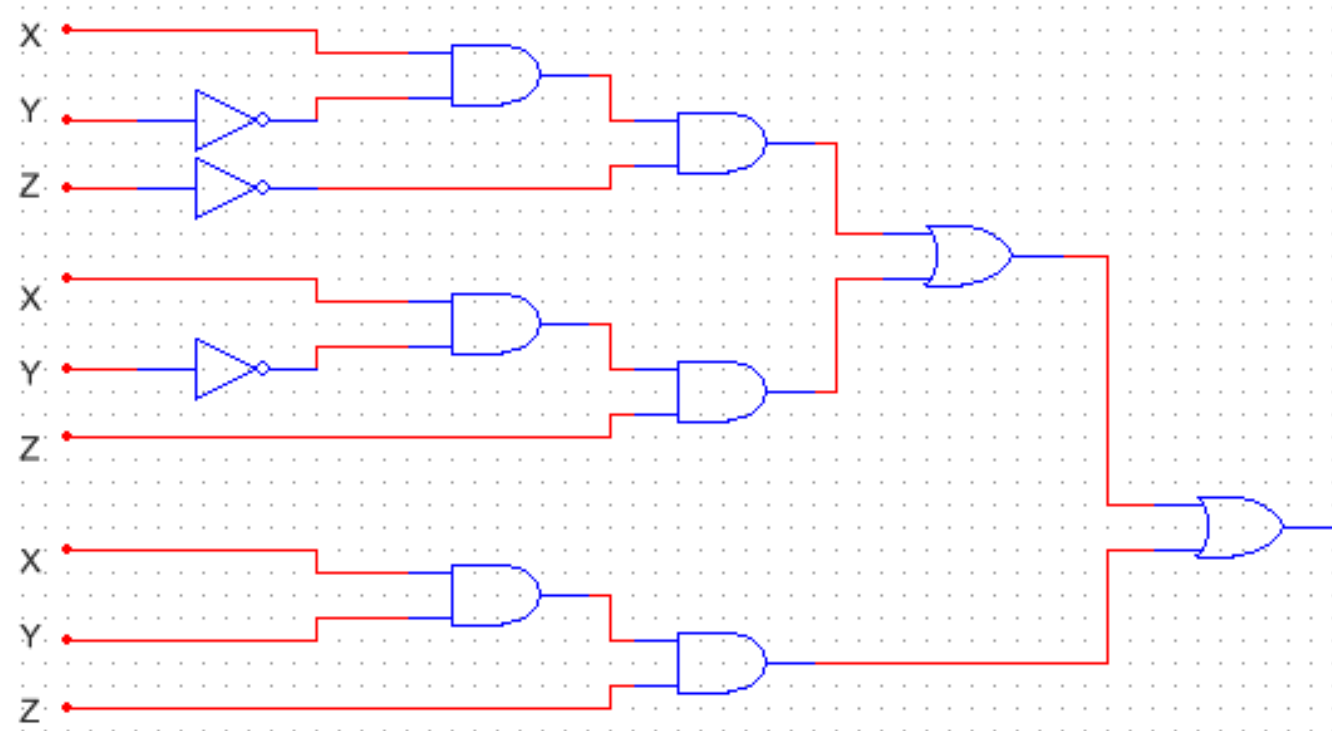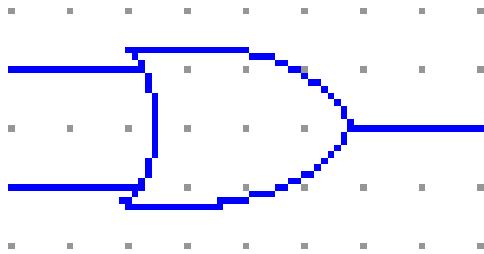
- 3) OR the min-terms to form the solution using an OR Gate


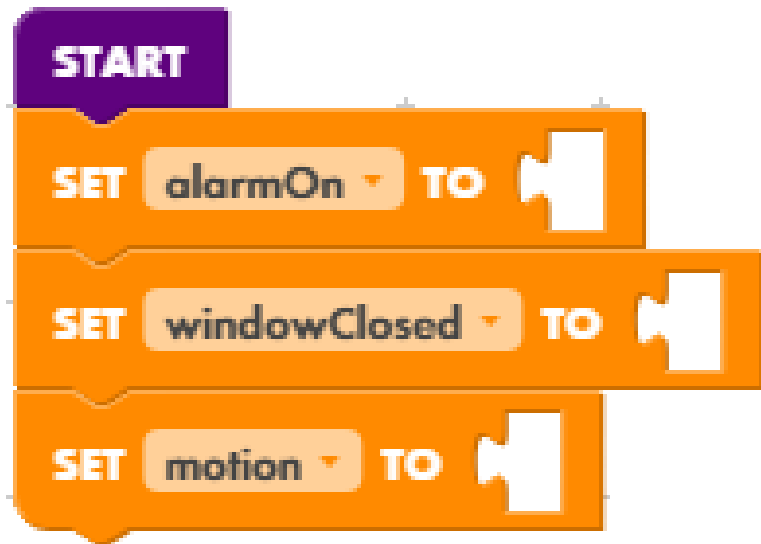
# Test the Solution (Software)

$$X\bar{Y}\bar{Z} + X\bar{Y}Z + XYZ$$

- o) Define variables for each input.  
A common practice is name the variable after the positive (true) state



```
logic circuit.py X
1 alarmOn = False
2 windowClosed = True
3 motion = True
```

# Test the Solution (Software)

---

$$X\bar{Y}\bar{Z} + X\bar{Y}Z + XYZ$$

- 1) Invert any inputs that have to be inverted using the inversion operator



```
not windowClosed  
not motion
```

# Test the Solution (Hardware)

$$X\bar{Y}\bar{Z} + X\bar{Y}Z + XYZ$$

- 2) AND the inputs to form a min-term using AND operators



```
alarmOn and not windowClosed and not motion
```


```
alarmOn and not windowClosed and motion
```

```
alarmOn and windowClosed and motion
```

# Test the Solution (Software)

$$X\bar{Y}\bar{Z} + X\bar{Y}Z + XYZ$$

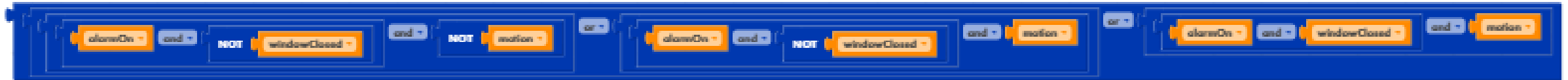- 3) OR the min-terms to form the solution using an OR Gate



```
(alarmOn and not windowClosed and not motion) or (alarmOn and not windowClosed and motion) or (alarmOn and windowClosed and motion)
```

# References

---

Digital Logic Circuits created in National Instruments Multisim

Block-Based Code created in littleBits Code Kit

Text-Based Code created in Notepad++